

Ladder Program:

AND GATE:



OR GATE:



NOR GATE:




EX-OR gate:




EX-NOR gate:



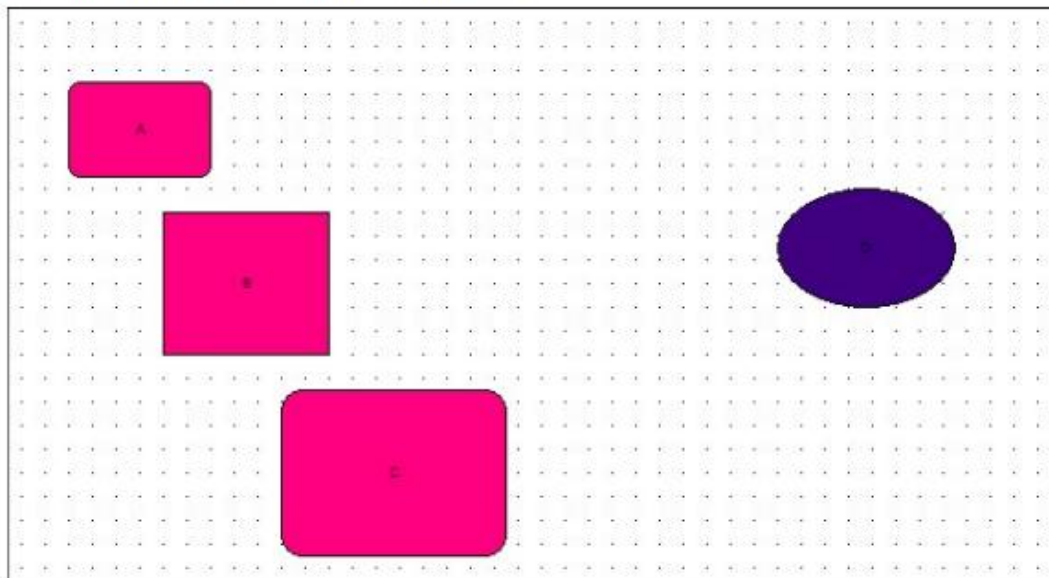
Visualization panel for a three input logical circuit.




Flow chart:

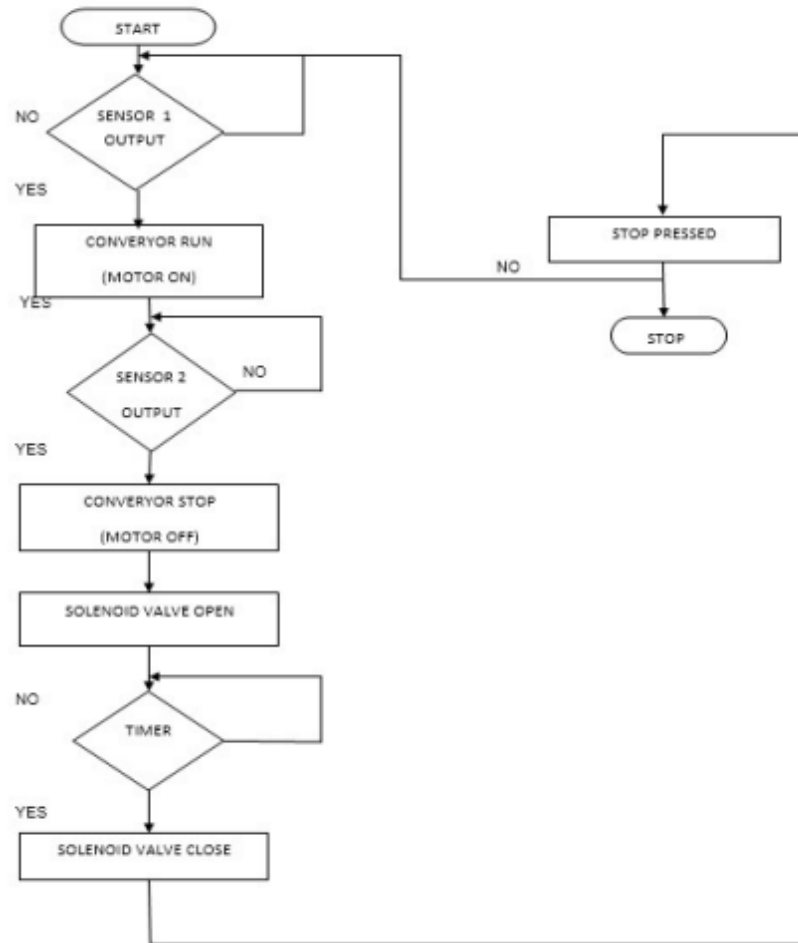

Ladder Diagram

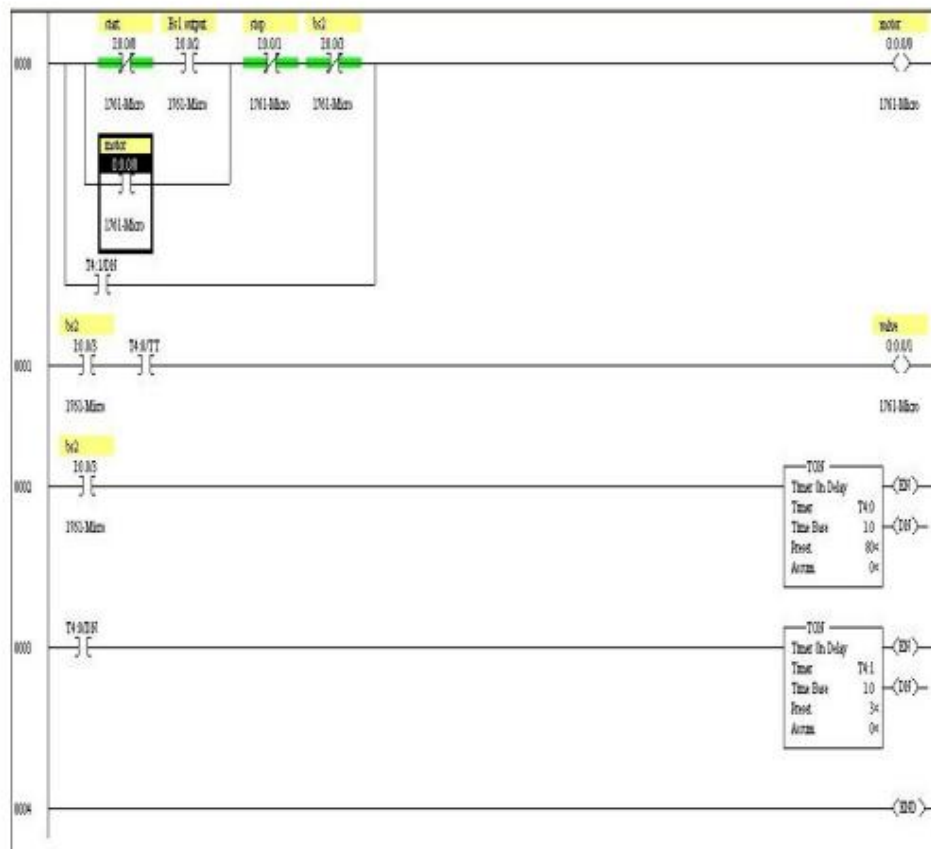


Ladder Diagram:

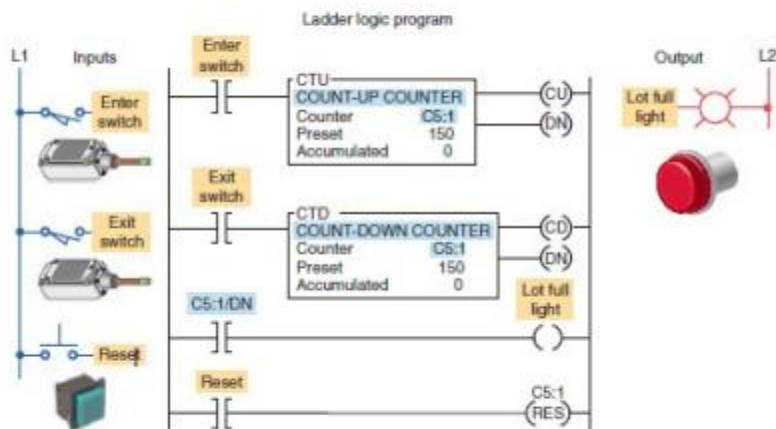

OUTPUT:

Red in north/south & green in east/west:

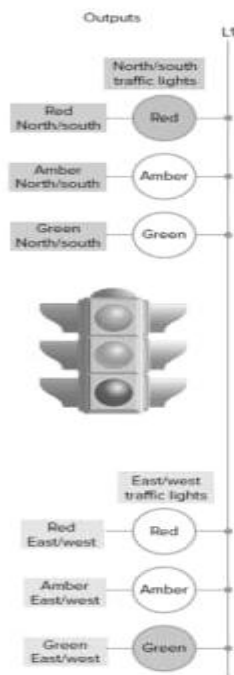


Green in north/south & red in east/west:



OUTPUT:

SIMULATION SETUP:

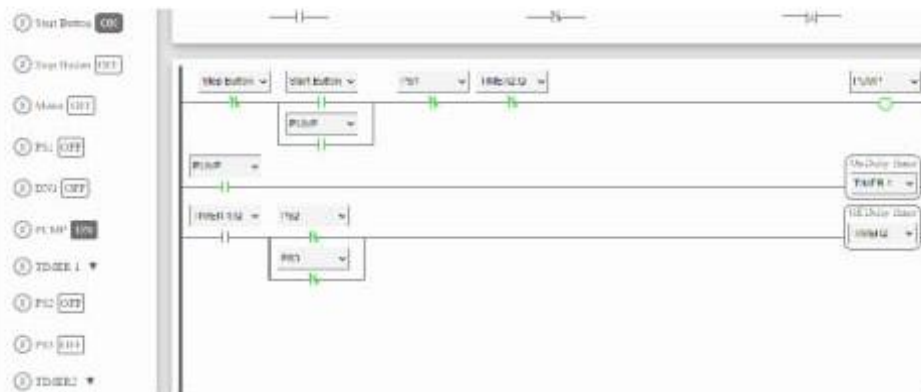

PUMP CONTROL:




Copy

Select all

Add comment



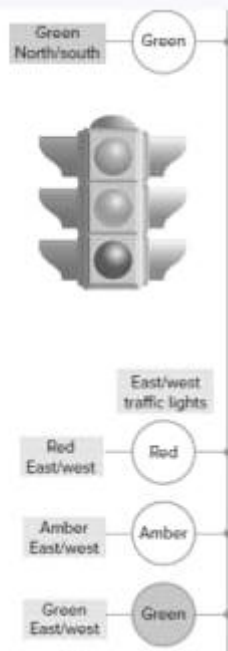

Green in north/south & red in east/west:

